
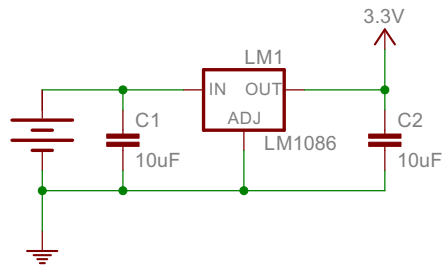




Voltage Regulator

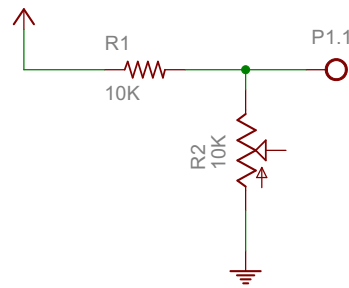

Left Motor Control



Right Motor Control

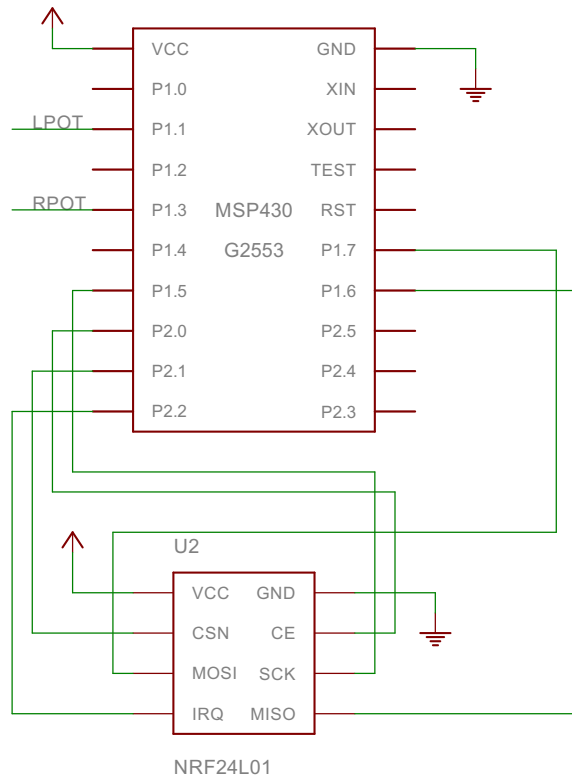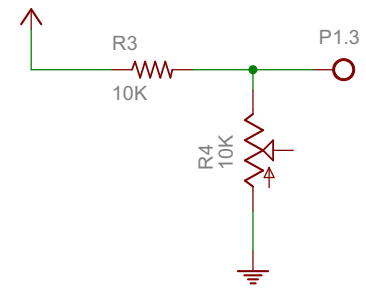

EE40 - Final Project: Remote Control

Authors: Aravind Kumaraguru, Scout Heid

Date: 12/10/14

Description: Remote control schematic

Page: 2/2